
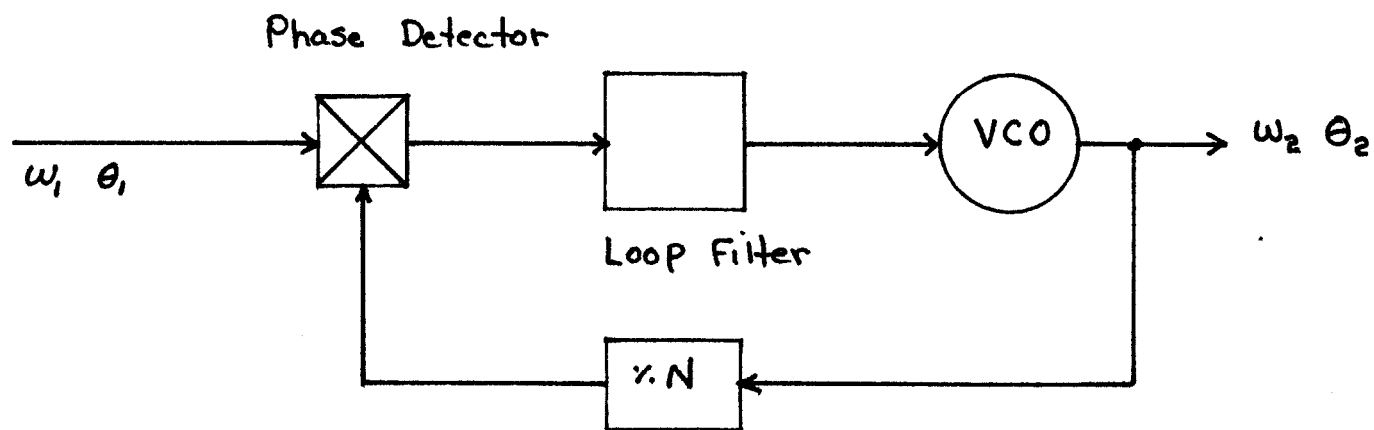


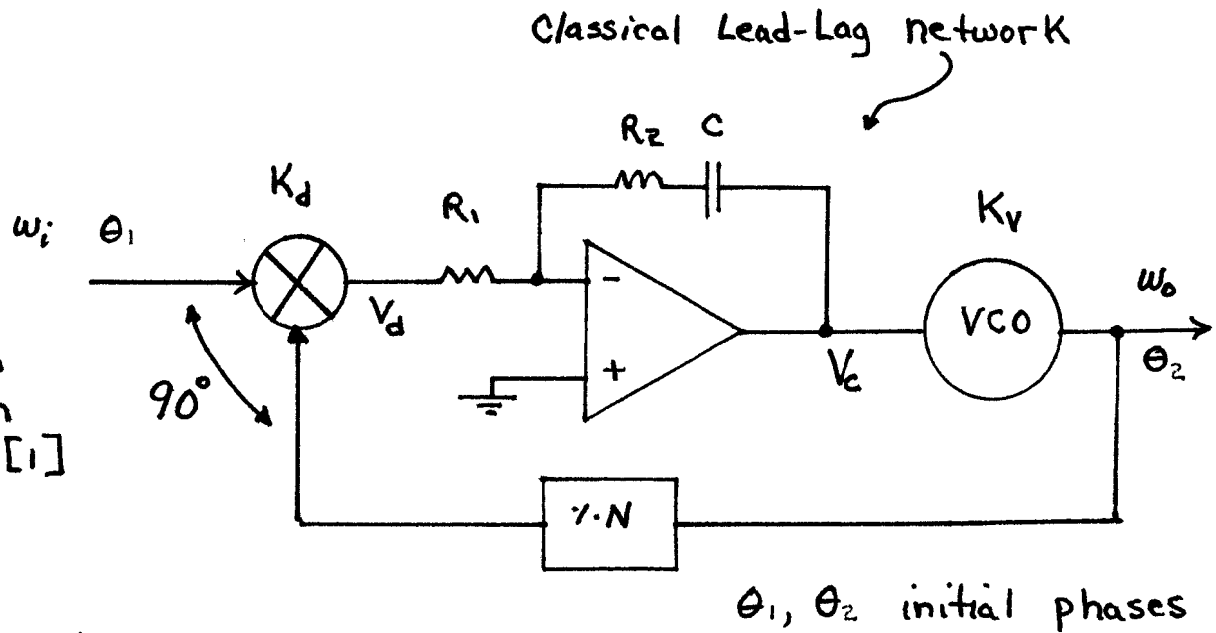The Phase-Locked Loop Concept for Frequency Synthesis



Consider a Type II PLL:

Loop Type: Number of ideal integrators in the open-loop gain transfer function [1]



Standard Servo-System Nomenclature:

Natural Frequency $\omega_n = \sqrt{\frac{K_d K_v}{N \gamma_1}}$


Damping Factor $\xi = \frac{1}{2} \omega_n \gamma_2$

Time Constants $\gamma_1 = R_1 C$
 $\gamma_2 = R_2 C$

Phasor Concept

At ϕ -det. :

$t \equiv 0$

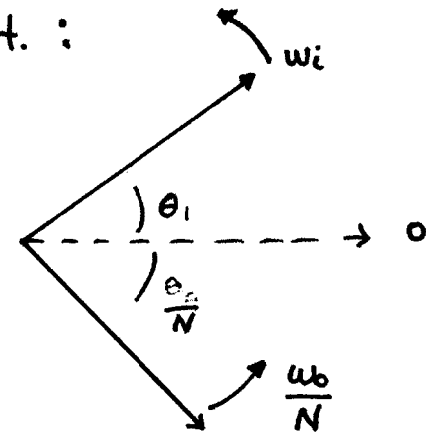

Time-Domain Analysis (Noise-Free Type II) [2]

The VCO acts as an ideal phase integrator:

$$\text{Total output phase } \theta_o = \omega_c t + \int_0^t K_V V_c dt + \theta_{oo}$$

$\omega_c =$ VCO center freq.

Assume $N=1$

$K_V =$ VCO sensitivity
Rad/sec/Volt

Mixer - Phase Detector

Multiplying inputs together and neglecting high frequency terms,

$$V_d = K_d \sin(\theta_i - \theta_o)$$

$\theta_i =$ total input phase

$$= K_d \sin \left[(\omega_i - \omega_c)t - \theta_{oo} - \int_0^t K_V V_c dt \right]$$

$= \omega_i t + 0$ (offset)

$$= K_d \sin \phi \quad \text{where } \phi = \theta_i - \theta_o$$

Lead-Lag Filter

Straight forward to show that

$$\gamma_1 \dot{V}_c = -V_d - \gamma_2 \dot{V}_d$$

Taking additional derivatives

$$\dot{\phi} = \dot{\theta}_i - \dot{\theta}_o = \omega_i - \omega_c - K_v V_c$$

$$\ddot{\phi} = -K_v \dot{V}_c = -\frac{K_v}{\tau_1} \left[V_d + \tau_2 \dot{V}_d \right]$$

$$\dot{V}_d = K_d \cos \phi \dot{\phi}$$


$$\ddot{\phi} = -\frac{K_v}{\tau_1} \left[K_d \sin \phi + \tau_2 K_d \cos \phi \dot{\phi} \right]$$

Hence

$$\frac{d^2 \phi}{dt^2} + \frac{K_d K_v \tau_2 \cos \phi}{\tau_1} \frac{d\phi}{dt} + \frac{K_d K_v \sin \phi}{\tau_1} \equiv 0 \quad \left\{ \begin{array}{l} \text{case of initial} \\ \text{phase \& freg. offset} \end{array} \right\}$$

Loop Analysis

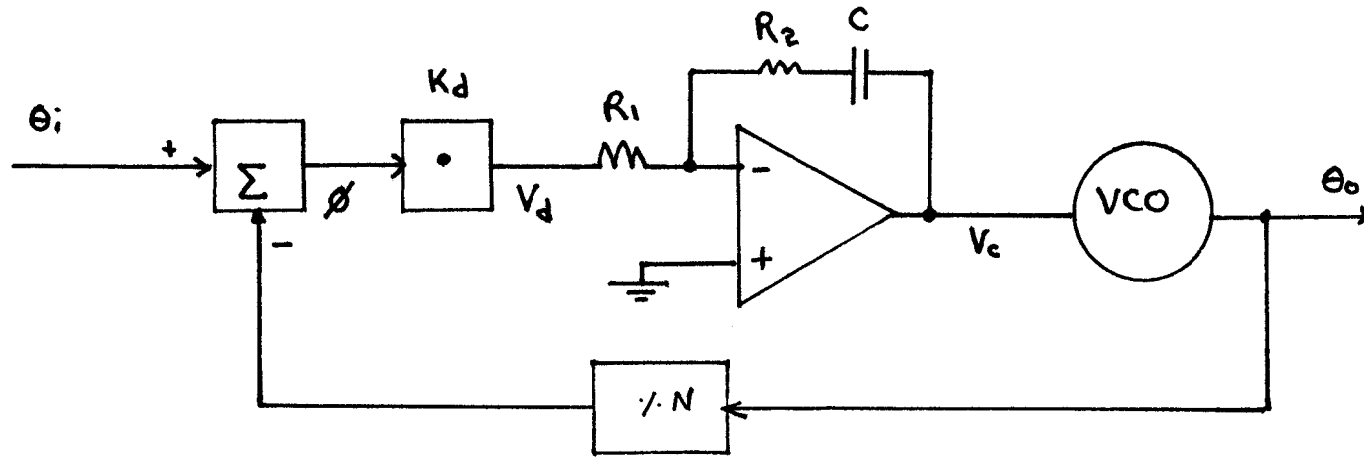Ideal Continuous Type II PLL (with linear approximation)



$$V_d = K_d \phi = K_d \left(\theta_i - \frac{\theta_o}{N} \right) = K_d \left[\theta_i - \frac{K_V}{SN} V_c(s) \right]$$

$$= K_d \left[\theta_i - \frac{K_V}{NS} \frac{1+s\tau_2}{s\tau_1} V_d \right]$$

$$V_d = \frac{K_d \theta_i}{1 + \frac{K_d K_V}{N \tau_1} \frac{1+s\tau_2}{s^2}}$$

$$\text{OR } \phi(s) = \frac{s^2 \theta_i(s)}{s^2 + \frac{K_d K_V \tau_2}{N \tau_1} s + \frac{K_d K_V}{N \tau_1}} = \frac{s^2 \theta_i(s)}{s^2 + 2\zeta \omega_n s + \omega_n^2}$$

$$\omega_n^2 = \frac{K_d K_V}{N \tau_1} \quad ; \quad \zeta = \frac{1}{2} \omega_n \tau_2$$

Important Synthesizer Specifications

- Bandwidth
- Channel Spacing
- Phase Noise
- Spurs
- Switching Speed
- Power Consumption
- Post-Tuning Drift
- EMI

Type II PLL Bandwidth Relationships [1]

0-dB open-loop BW $\omega_{0dB} = \omega_n \left[2\zeta^2 + \sqrt{4\zeta^4 + 1} \right]^{1/2}$

3dB closed-loop BW $\omega_{3dB} = \omega_n \left[1 + 2\zeta^2 + \sqrt{(2\zeta^2 + 1)^2 + 1} \right]^{1/2}$

Phase Margin $\phi_m = \tan^{-1} \left[\frac{2\omega_0 \zeta}{\omega_n} \right]$

where $\omega_0 = \omega_n \left[2\zeta^2 + \sqrt{4\zeta^4 + 1} \right]^{1/2}$



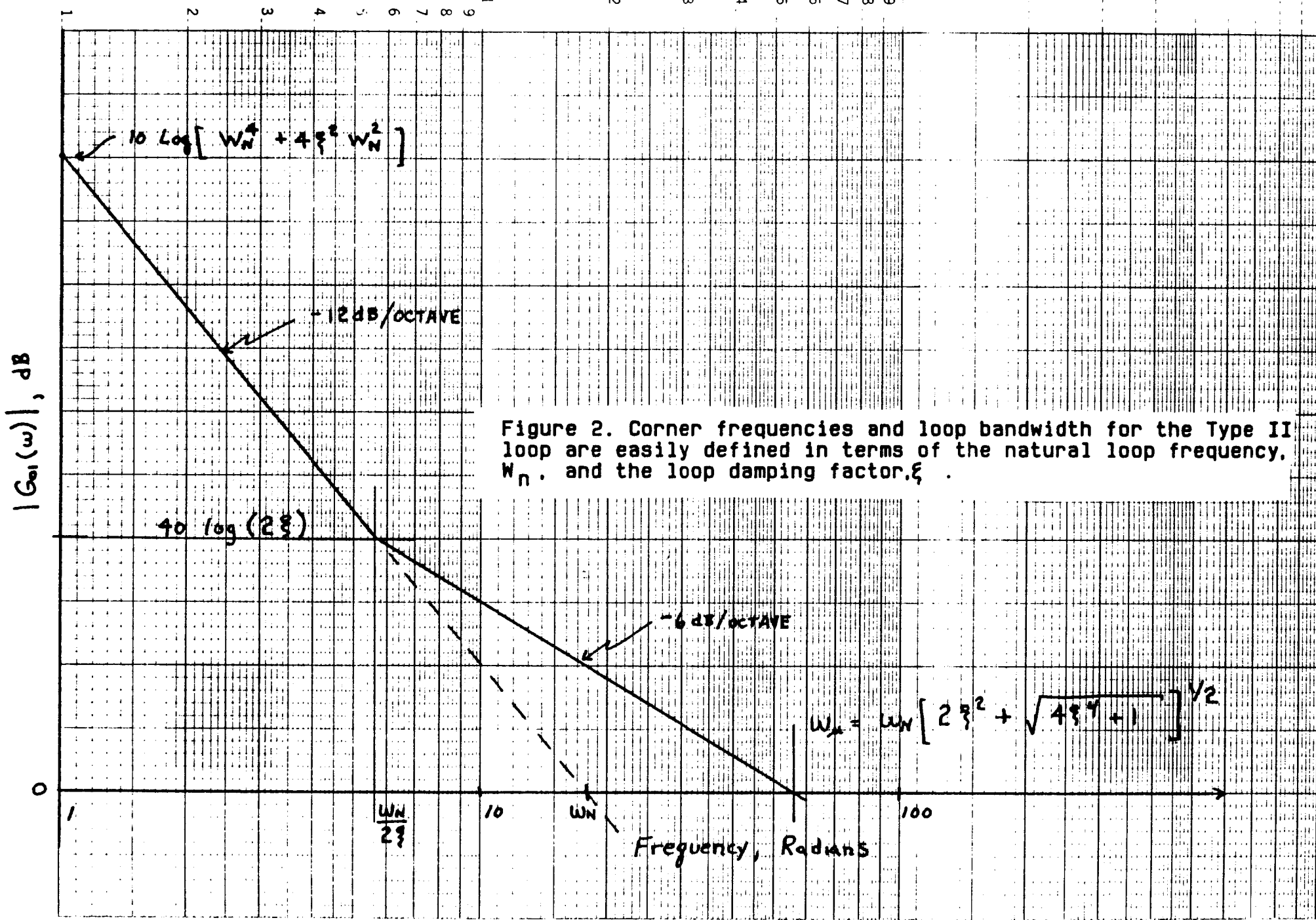


Figure 2. Corner frequencies and loop bandwidth for the Type II loop are easily defined in terms of the natural loop frequency, ω_n , and the loop damping factor, ξ .

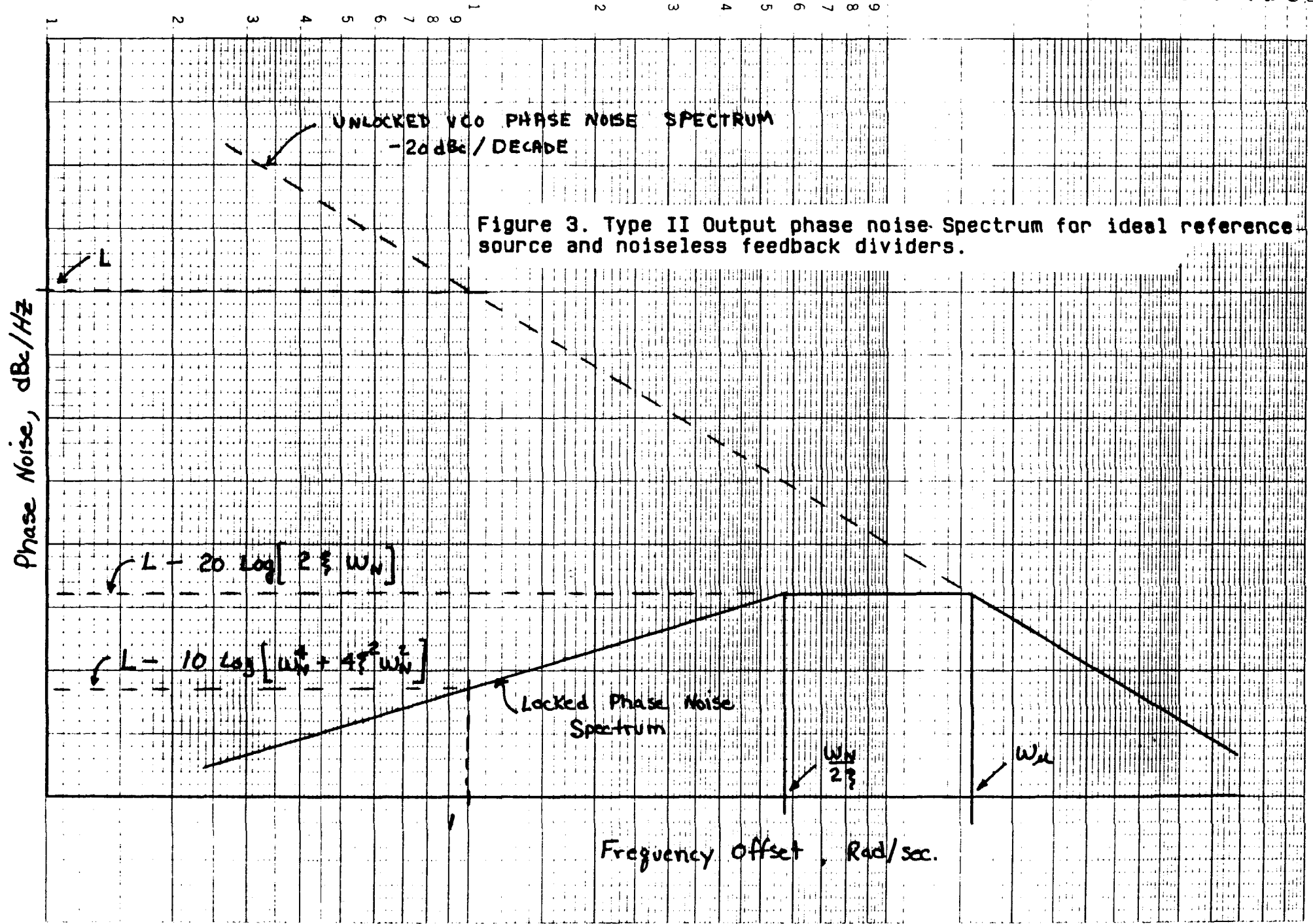

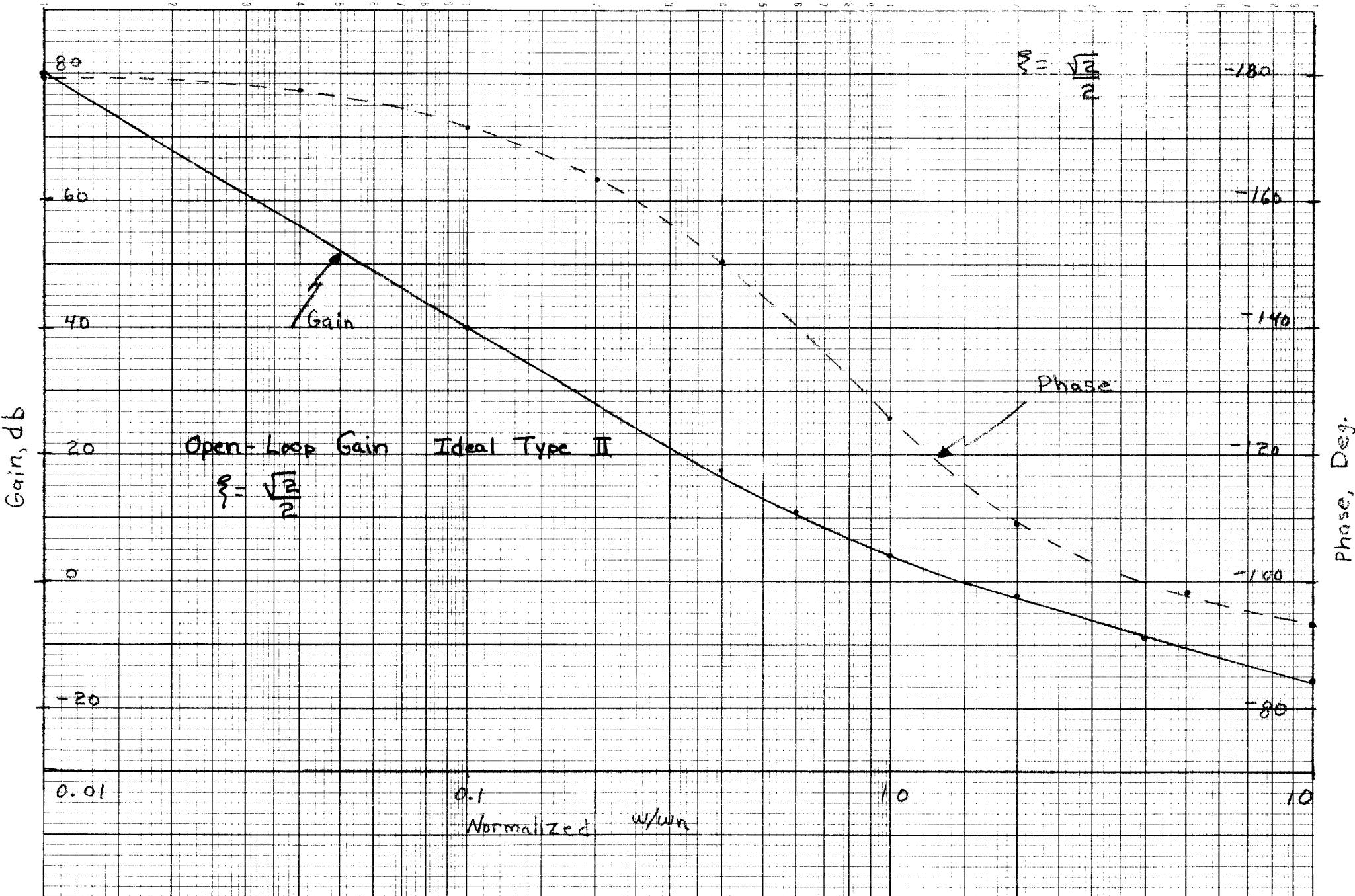

From:

"Noise Property Analysis Enhances PLL Designs"

Larry Martin
EDN Sept. 16, 1981

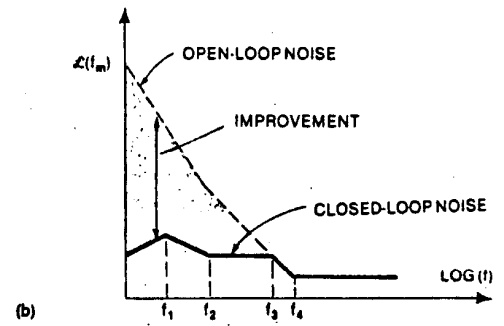
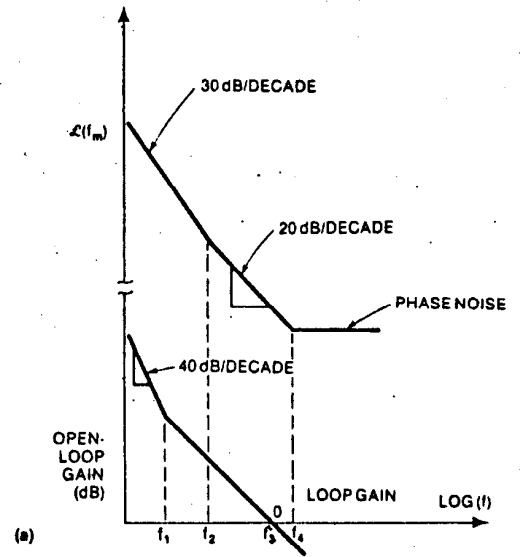


Fig 6—These Bode plots of open-loop phase noise and gain (a) and closed-loop VCO noise (b) show the reduction of oscillator phase noise inside the loop bandwidth by the available loop gain at any offset frequency.

From :

"Noise Property Analysis Enhances PLL Designs"

Larry Martin

EDN Sept. 16, 1981

NOISE DATA

OFFSET FREQUENCY (Hz)	$\mathcal{L}(f_m)$		
	VCO (dBc)	REFERENCE (dBc)	DIVIDER (dBc)
10	22	87	99
100	52	92	115
1000	82	97	124
10,000	112	102	127
100,000	132	102	147

$$\overline{e_{VT}} = 30 \text{ nV}/\sqrt{\text{Hz}}$$

$$K_p = [0.4/(2\pi)] \text{ V/RAD}$$

$$N = 240$$

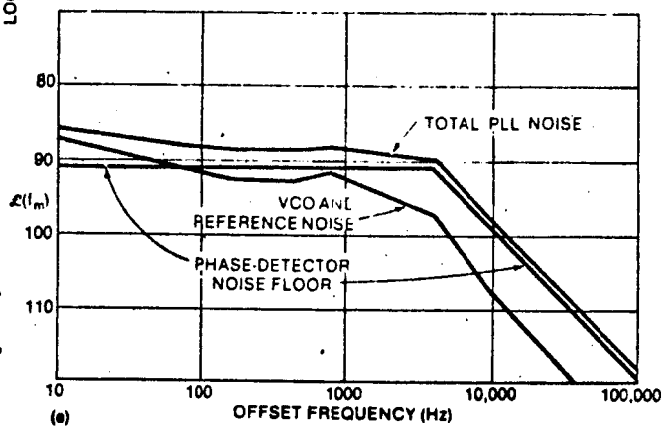
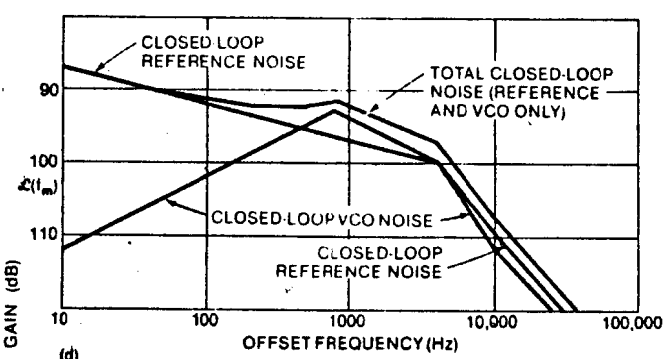
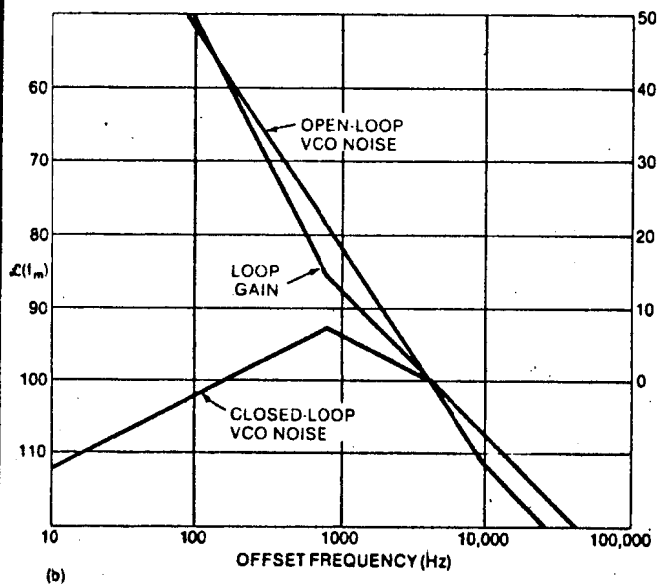
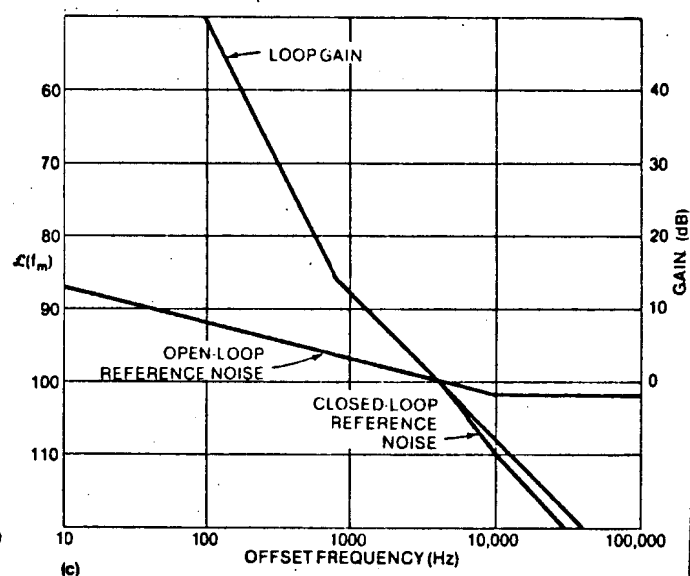
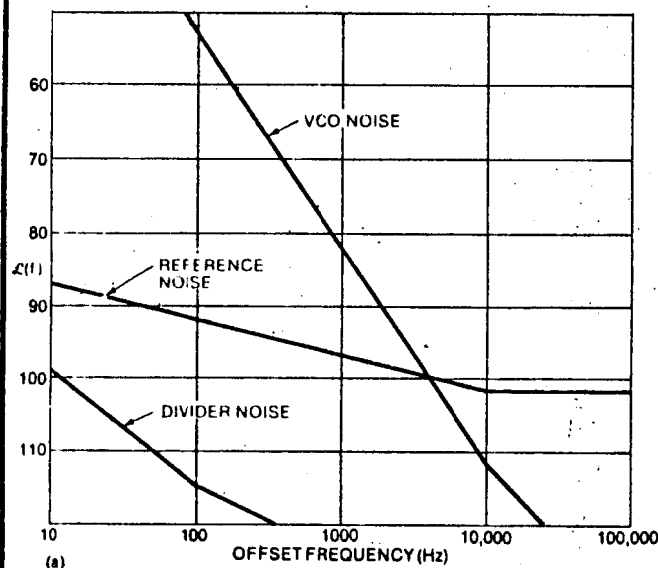


Fig 9—These curves illustrate the noise characteristics of the individual components in Fig 8 as well as the resulting total noise. (a) shows VCO, divider and frequency-reference phase noise; (b), loop gain and VCO noise; (c), loop gain and reference noise; (d), total closed-loop noise due to the reference and VCO noise; (e), total PLL noise.

Table 4.1 Transient Phase Error of Second-Order Loop, $\theta_e(t)$ (in rad) (high loop gain; $K_v K_d \gg \omega_n$)

	Phase Step ($\Delta\theta$ rad)	Frequency Step ($\Delta\omega$ rad/sec)	Frequency Ramp ($\Delta\dot{\omega}$ rad/sec ²)
$\zeta < 1$	$\Delta\theta \left(\cos \sqrt{1-\zeta^2} \omega_n t - \frac{\zeta}{\sqrt{1-\zeta^2}} \sin \sqrt{1-\zeta^2} \omega_n t \right) e^{-\zeta\omega_n t}$	$\frac{\Delta\omega}{\omega_n} \left(\frac{1}{\sqrt{1-\zeta^2}} \sin \sqrt{1-\zeta^2} \omega_n t \right) e^{-\zeta\omega_n t}$	$\frac{\Delta\dot{\omega}}{\omega_n^2} - \frac{\Delta\dot{\omega}}{\omega_n^2} \left(\cos \sqrt{1-\zeta^2} \omega_n t + \frac{\zeta}{\sqrt{1-\zeta^2}} \sin \sqrt{1-\zeta^2} \omega_n t \right) e^{-\zeta\omega_n t}$
$\zeta = 1$	$\Delta\theta (1 - \omega_n t) e^{-\omega_n t}$	$\frac{\Delta\omega}{\omega_n} (\omega_n t) e^{-\omega_n t}$	$\frac{\Delta\dot{\omega}}{\omega_n^2} - \frac{\Delta\dot{\omega}}{\omega_n^2} (1 + \omega_n t) e^{-\omega_n t}$
$\zeta > 1$	$\Delta\theta \left(\cosh \sqrt{\zeta^2-1} \omega_n t - \frac{\zeta}{\sqrt{\zeta^2-1}} \sinh \sqrt{\zeta^2-1} \omega_n t \right) e^{-\zeta\omega_n t}$	$\frac{\Delta\omega}{\omega_n} \left(\frac{1}{\sqrt{\zeta^2-1}} \sinh \sqrt{\zeta^2-1} \omega_n t \right) e^{-\zeta\omega_n t}$	$\frac{\Delta\dot{\omega}}{\omega_n^2} - \frac{\Delta\dot{\omega}}{\omega_n^2} \left(\cosh \sqrt{\zeta^2-1} \omega_n t + \frac{\zeta}{\sqrt{\zeta^2-1}} \sinh \sqrt{\zeta^2-1} \omega_n t \right) e^{-\zeta\omega_n t}$
	Steady-state error = 0	Steady-state error = $\frac{\Delta\omega}{K_v}$ (not included above)	Steady state error = $\frac{\Delta\dot{\omega}t}{K_v} + \frac{\Delta\dot{\omega}}{\omega_n^2}$ ($\Delta\dot{\omega}t/K_v$ not included above)

From Gardner [1]

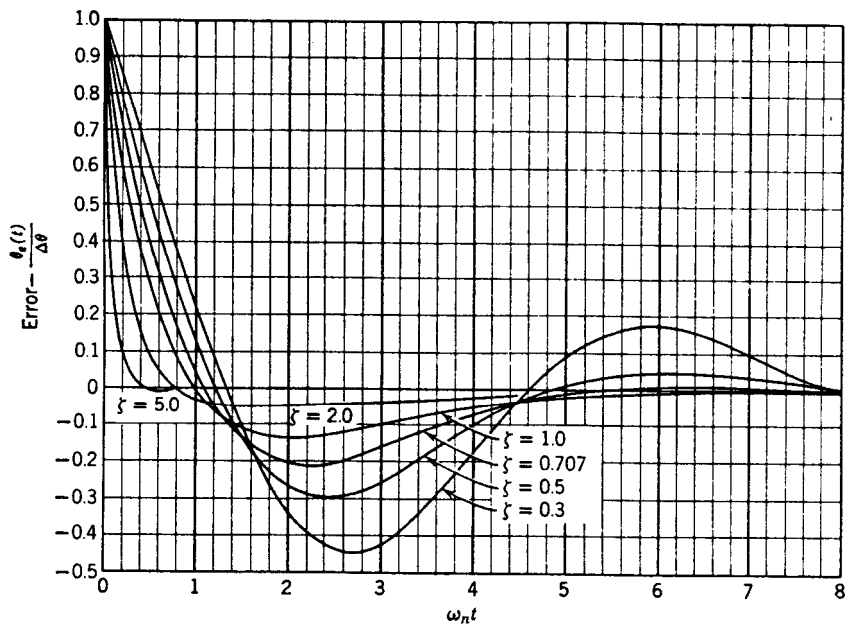


Figure 4.1 Phase error $\theta_e(t)$ due to a step in phase $\Delta\theta$. From Ref. 1 by permission of L. A. Hoffman.




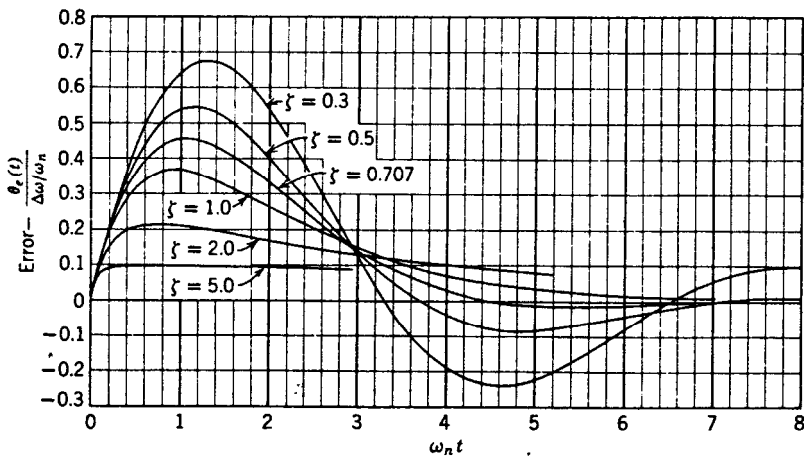


Figure 4.2 Transient phase error $\theta_e(t)$ due to a step in frequency $\Delta\omega$. (Steady-state velocity error, $\Delta\omega/K_v$, neglected.) From Ref. 1 by permission of L. A. Hoffman.

From Gardner
[1]

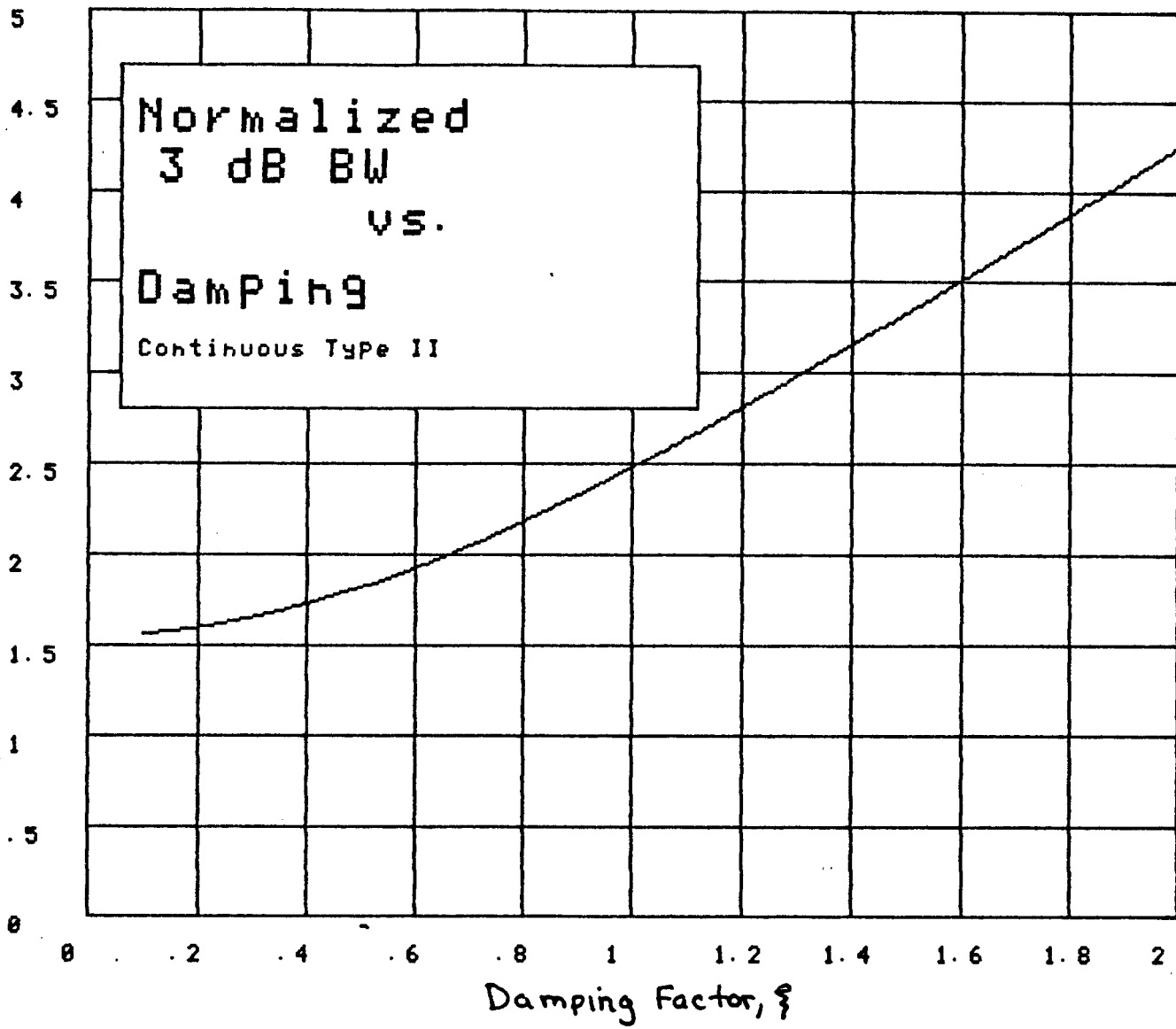

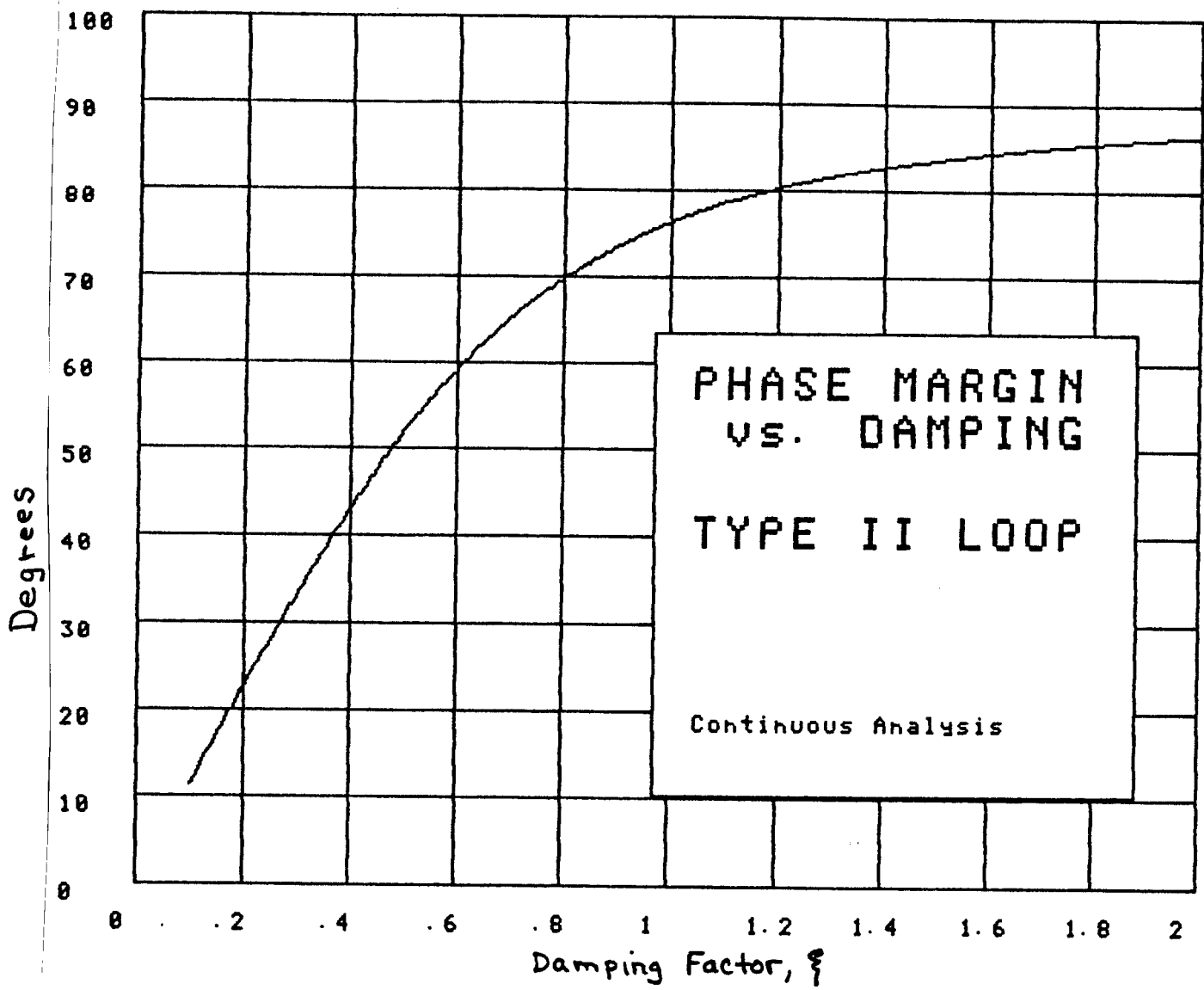

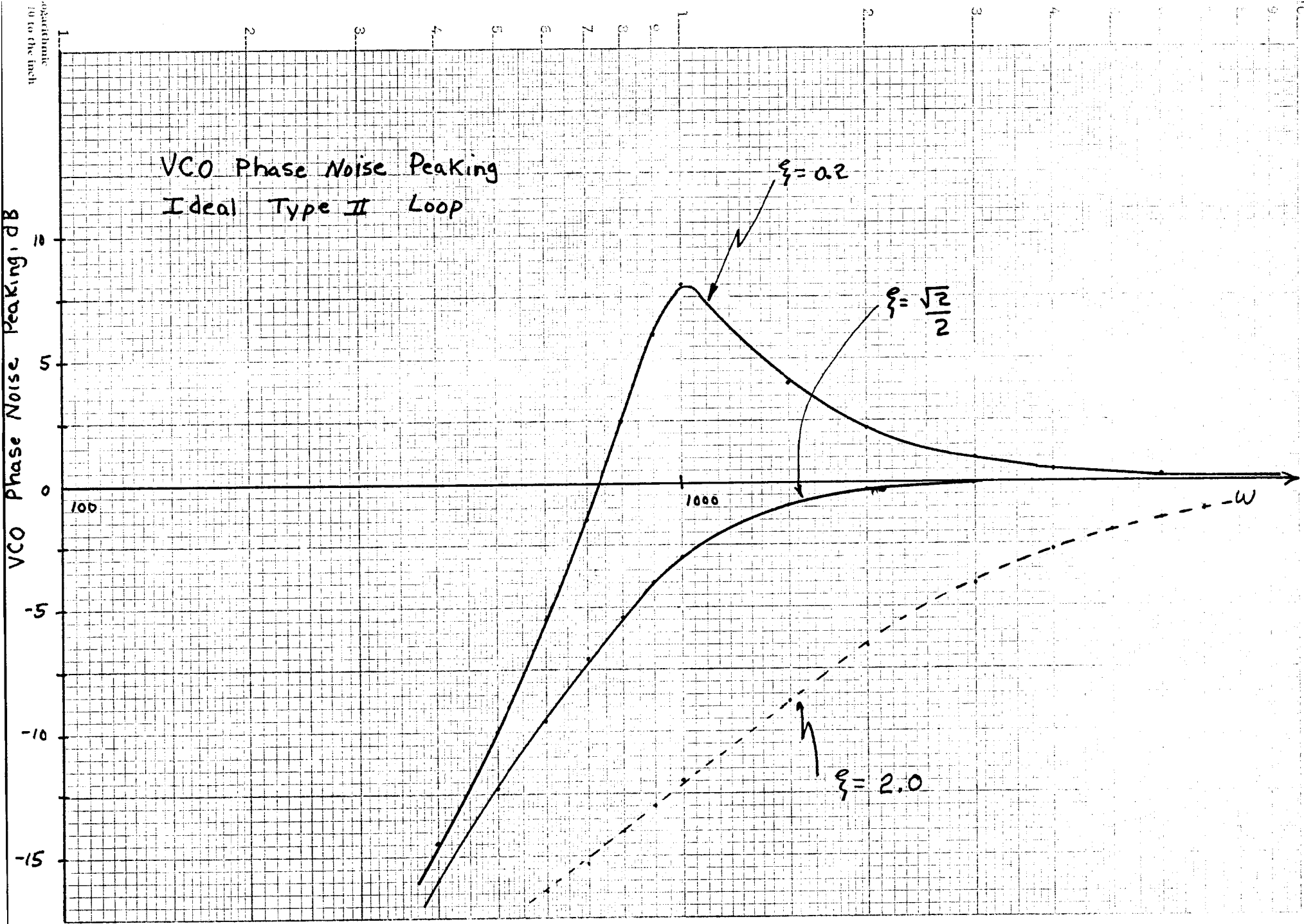

Phase Noise Transfer Functions

Ideal Type II, I PLL

Loop Type

Divider

VCO

I

$$\frac{N \theta_d(s)}{1 + s/W_N}$$

$$\frac{\theta_v(s) s/W_N}{1 + s/W_N}$$

II

$$\frac{\theta_d(s) N (1 + 2s^2/W_N)}{1 + 2s^2/W_N + (s/W_N)^2}$$

$$\frac{\theta_v(s) (s/W_N)^2}{1 + 2s^2/W_N + (s/W_N)^2}$$

Internal Loop Transport Delay

Open-loop Gain Function $G_{OL}(s) = \omega_n^2 \frac{(1 + 2\zeta s/\omega_n)}{s^2} \underbrace{e^{-s\tau_d}}_{\text{Delay Term}}$

Excellent 1st Order Approx $G_{OL}(s) = \omega_n^2 \frac{(1 + 2\zeta s/\omega_n)}{s^2} \frac{1}{1 + s\tau_d}$

Case: Step Change in Frequency

No closed-form solution possible for exact Type II case.

Solution for exact Type I loop with delay:

$$\theta_E(t) = \frac{2\pi \Delta f}{N} \left[t + \sum_{n=1}^{\frac{t}{\tau} = N} (-\omega_n)^n \frac{(t - n\tau)^{n+1}}{(n+1)!} u(t - n\tau) \right]$$

Time delay is always detrimental to achievable switching speed and phase noise.

$|G_{OL}|, \text{dB}$

$\propto 20 \log(\omega_N)$

-6dB/octave

Open-loop gain
Ideal Type I

-180

-160

-140


Phase, deg


-110

-90


Frequency, ω

1

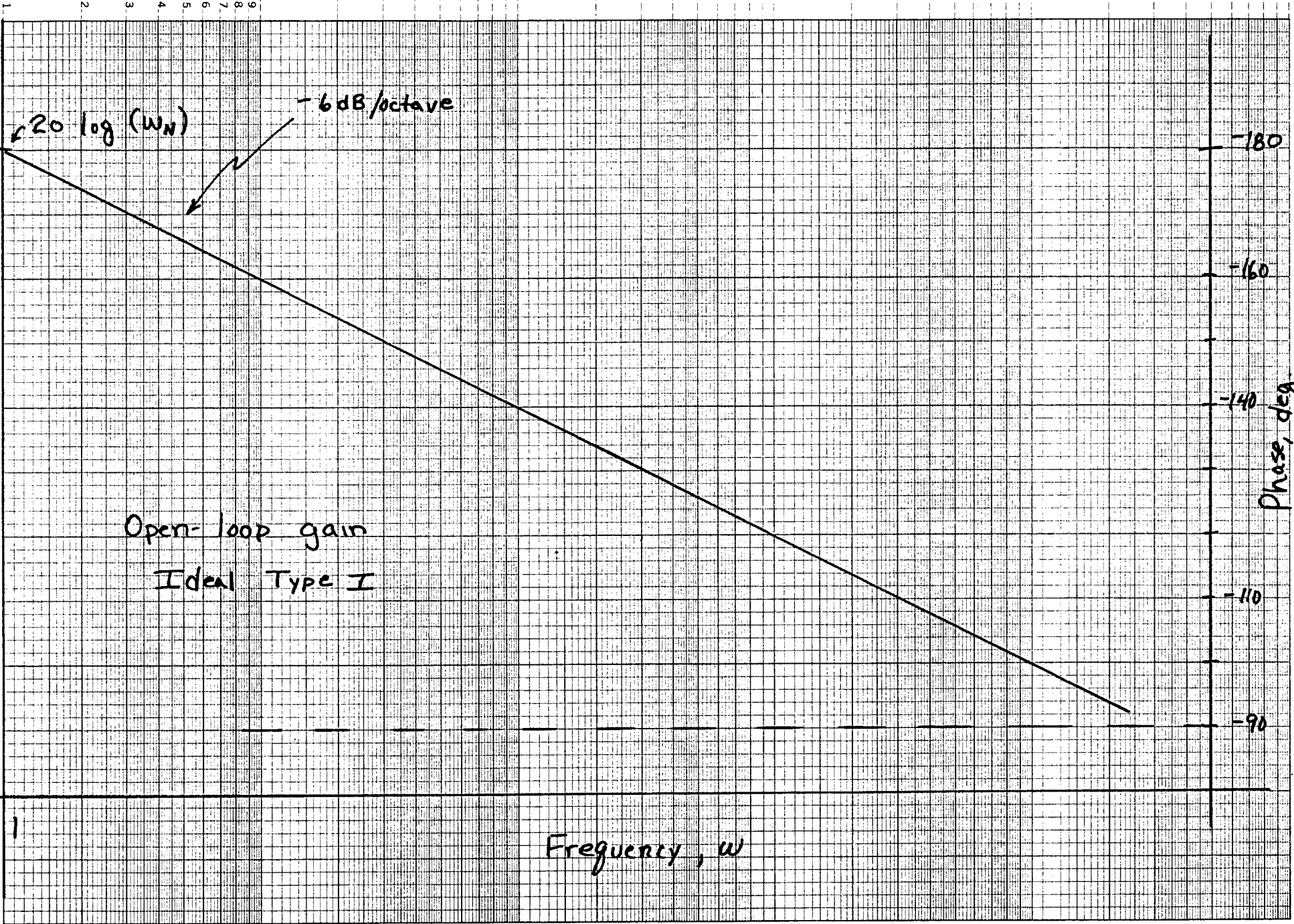

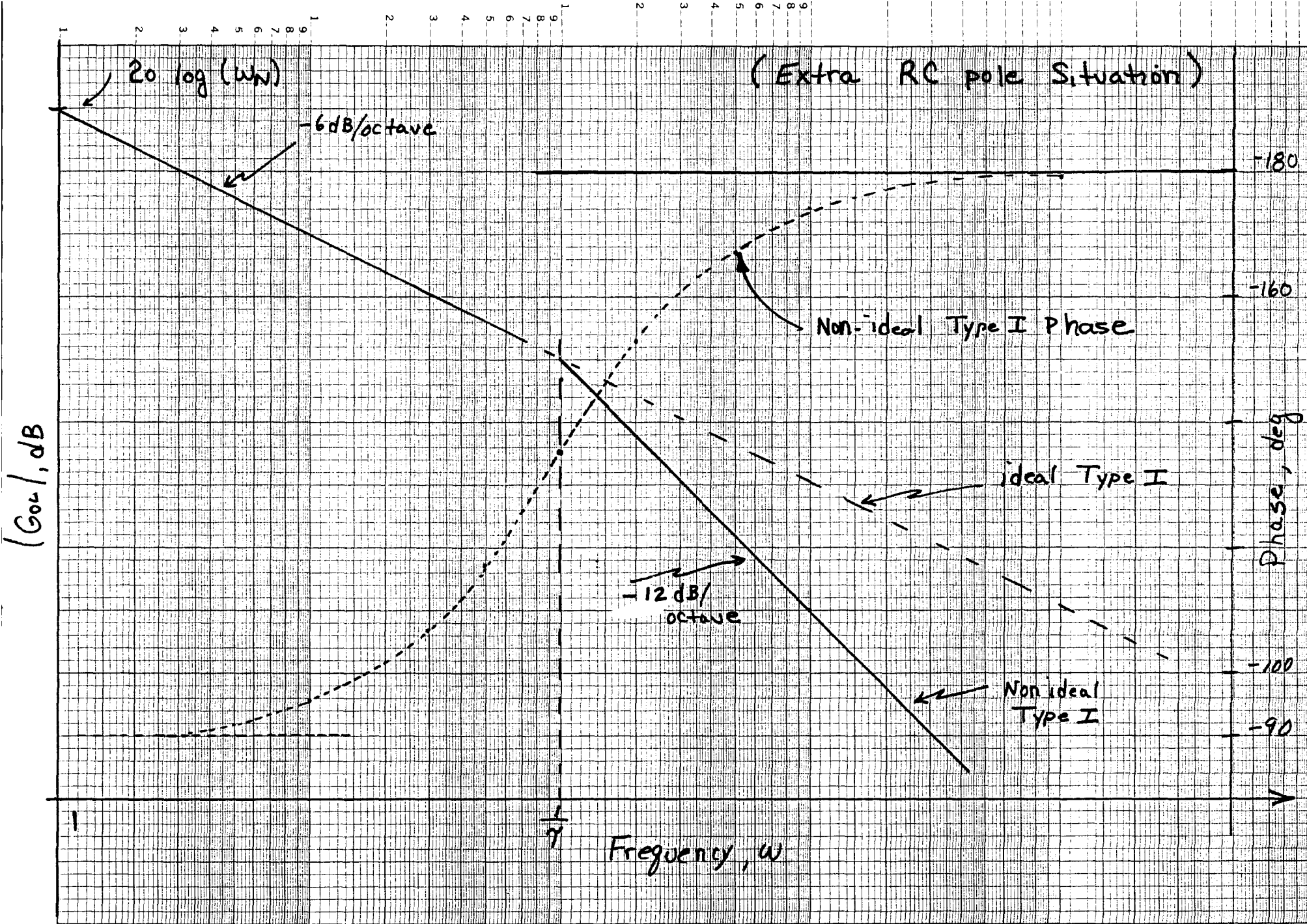

Secret-Logarithmic
Circle 10 to the inch

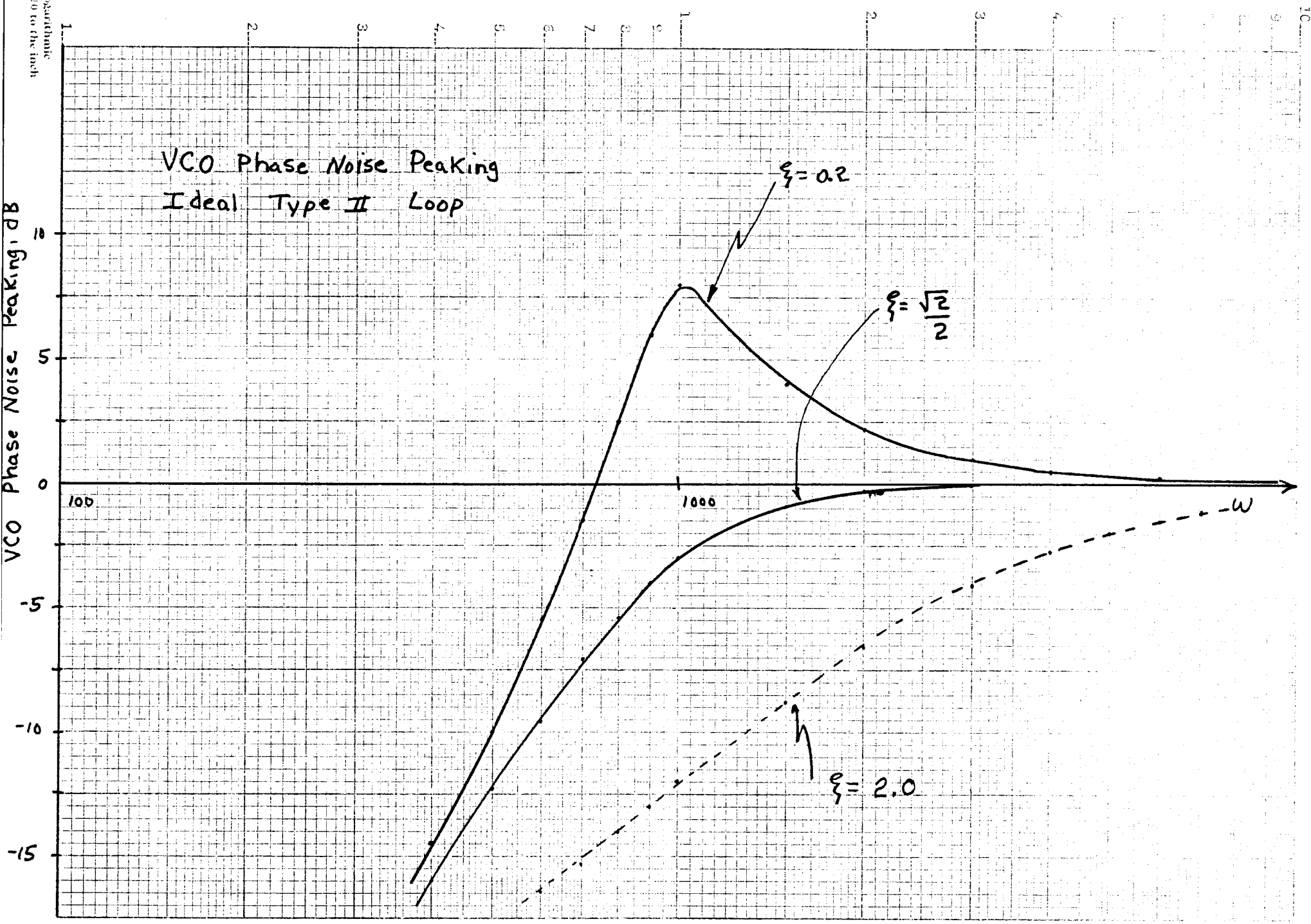

Oscillator Phase Noise Models

Leeson [3]

$$S_{\phi}(f_m) = \frac{F K T}{P_o} \left[1 + \left(\frac{f_o}{2Q f_m} \right)^2 \right]$$

Haggai

$$S_{\phi}(f_m) = \frac{\epsilon}{\pi B_c} \frac{1}{1 + \left(\frac{2 f_m}{B_c} \right)^2}$$

$$B_c = \frac{\pi}{2} \frac{F K T}{P_o} \left(\frac{f_o}{Q} \right)^2$$

F	noise factor
T	Absolute Temp
f _o	Center Frequency
Q	Loaded Q
P _o	Power out
f _m	Offset frequency

(Equivalent Models)

Spectral Relationships for Wide-Sense Stationary Processes [4]

$$\left. \begin{aligned} S_{\phi}(\omega) &= \int_{-\infty}^{\infty} R_{\phi}(\tau) e^{-j\omega\tau} d\tau \\ R_{\phi}(\tau) &= \frac{1}{2\pi} \int_{-\infty}^{\infty} S_{\phi}(\omega) e^{j\omega\tau} d\omega \end{aligned} \right\} \text{W. K. Theorem}$$

Variance of Average Frequency Departure

$$\begin{aligned} \sigma^2 \left[\left\langle \dot{\phi} \right\rangle_{t, \tau} \right] &= \frac{2}{\tau^2} \left[R_{\phi}(0) - R_{\phi}(\tau) \right] \\ &= \frac{2}{\pi \tau^2} \int_{-\infty}^{\infty} S_{\phi}(\omega) \sin^2 \left(\frac{\omega\tau}{2} \right) d\omega \end{aligned}$$

Variance of Phase

$$\sigma^2 [\phi(t)] = R_{\phi}(0) = \frac{1}{2\pi} \int_{-\infty}^{\infty} S_{\phi}(\omega) d\omega$$

Variance of Accumulated Phase

$$\sigma^2 [\Delta_{\tau} \phi] = 2 \left[R_{\phi}(0) - R_{\phi}(\tau) \right]$$

Why Sampled Phase-Locked Loops?

- Any PLL which includes a divide-by- N in the feedback path is fundamentally a sampled system.
- Exclusion of sampled aspects in large bandwidth PLL's results in considerable error.
- Sampled PLL's are capable of faster switching speed per unit loop-bandwidth than any continuous PLL of the same type.


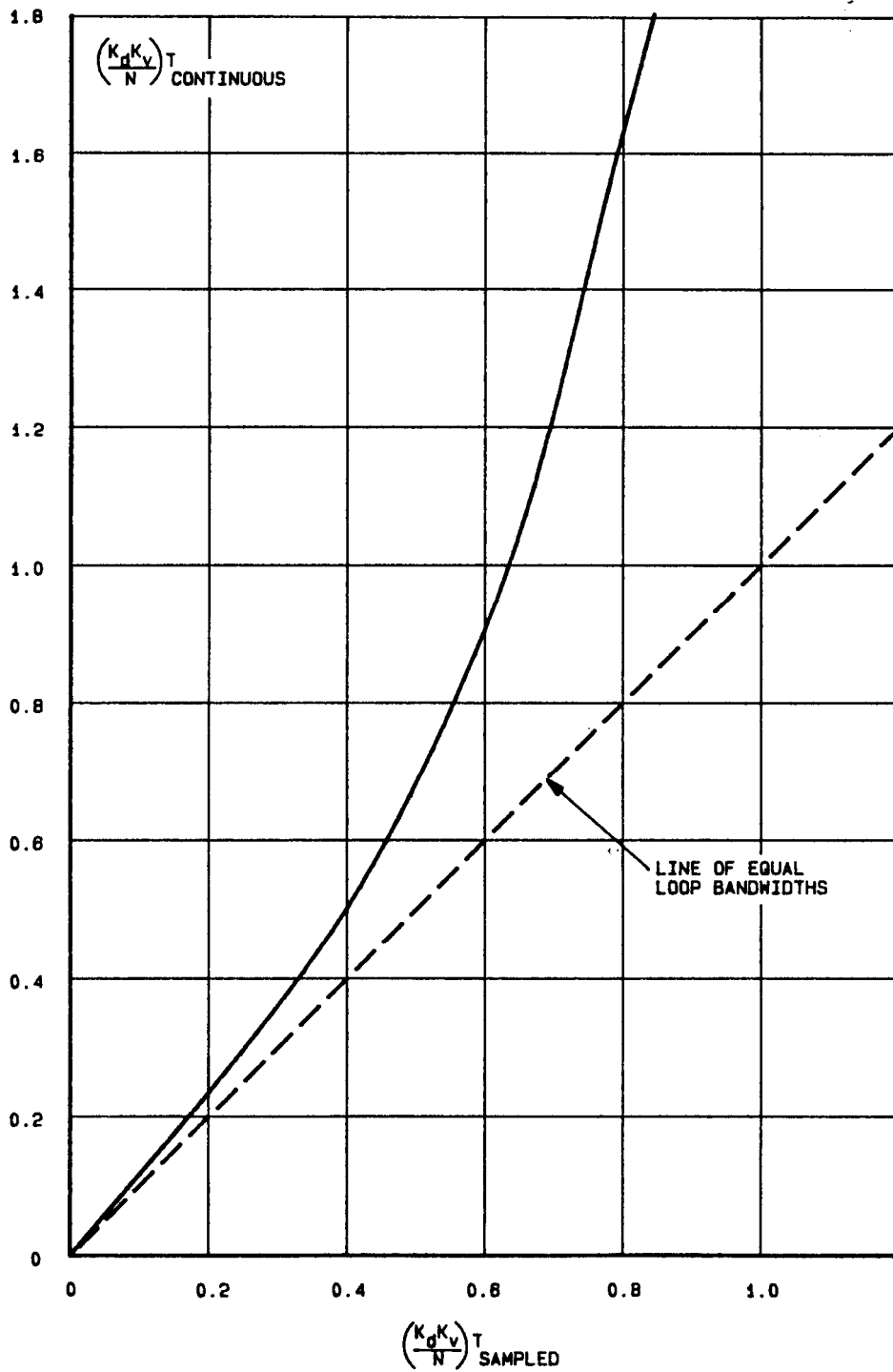


Figure 5. Continuous and Sampled Control System:
Phase-Locking Speed [s]



Sampled PLL Model

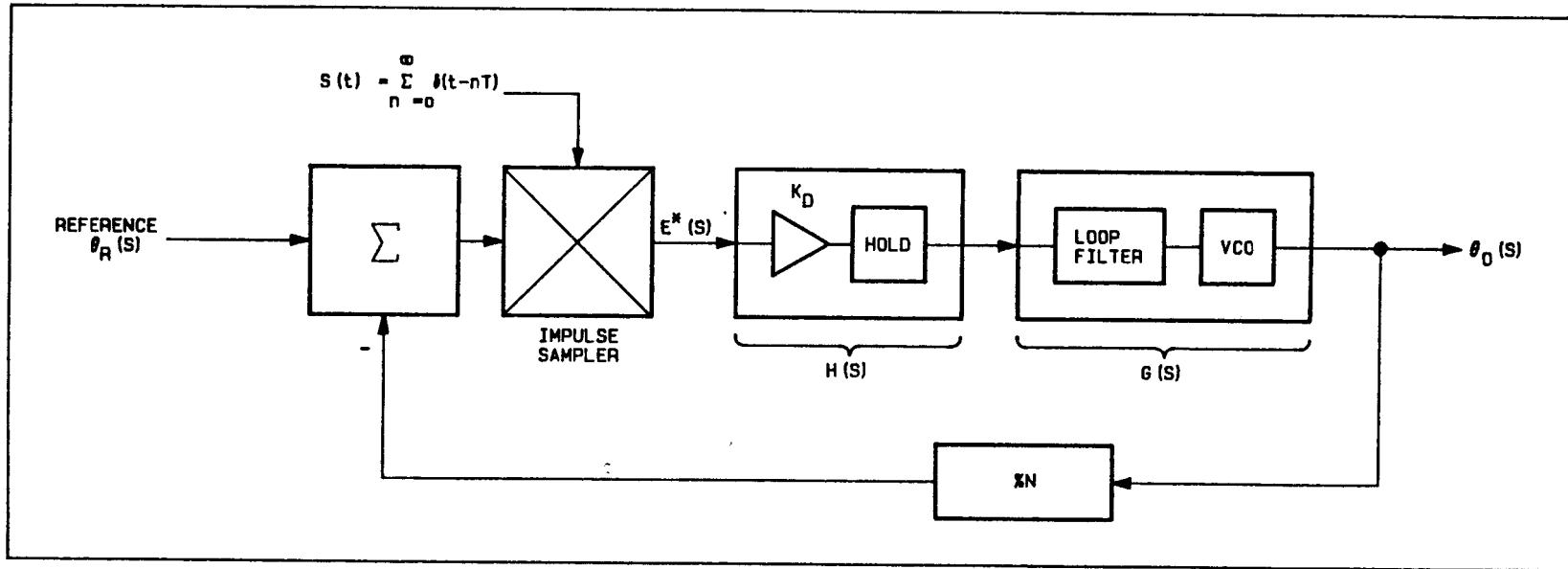

39184-4

Figure 4. The general Sampled phase-locked loop employs an ideal impulse Sampler which must be followed by some form of 'hold' device, $H(s)$ [s]

Prelude to Sampled Control Systems

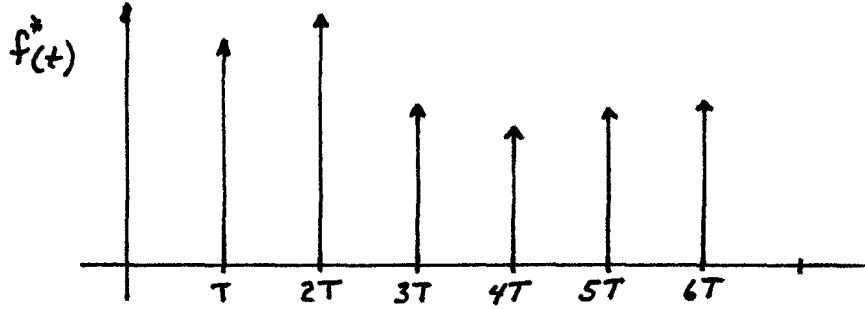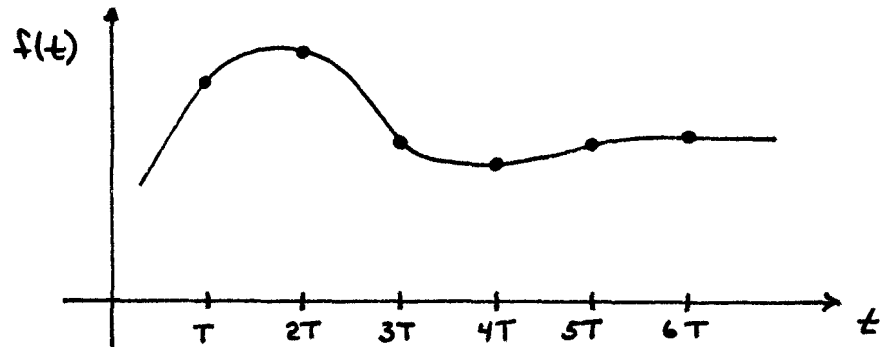

$$\mathcal{L}\{f^*(t)\} = \sum_{n=0}^{\infty} f(nT) e^{-sTn}$$
$$\equiv F(z)$$

Dirac Delta Functions

1) Unit Area $\int_{-\infty}^{\infty} \delta(t) dt = 1$

2) Sampling $\int_{-\infty}^{\infty} f(t) \delta(t-a) dt = f(a)$

Periodic Impulse Sampler

$$p(t) = \sum_{n=-\infty}^{\infty} \delta(t-nT)$$
$$= \frac{1}{T} \sum_{n=-\infty}^{\infty} e^{jn\omega_s t}$$

$$f^*(t) = f(t) p(t)$$
$$= f(t) \frac{1}{T} \sum_{n=-\infty}^{\infty} e^{jn\omega_s t}$$

$$\therefore \mathcal{F}\{f^*(t)\} = F^*(\omega) = \frac{1}{T} \sum_{n=-\infty}^{\infty} F(\omega - \omega_s n)$$

Sampled PLL Analysis : Error Response [s]

$$\begin{aligned} E^*(s) &= \left[\Theta_R(s) - \frac{\Theta_o(s)}{N} \right]^* \\ &= \left[\Theta_R(s) - \frac{E^*(s) G(s) H(s)}{N} \right]^* \\ &= \Theta_R^*(s) - \frac{E^*(s) G^*(s) H^*(s)}{N} \end{aligned}$$

$$\begin{aligned} E^*(s) &= \frac{\Theta_R^*(s)}{1 + \frac{G^*(s) H^*(s)}{N}} \\ &= \frac{\frac{1}{T} \sum_{n=-\infty}^{\infty} \Theta_R(s - jn\omega_s)}{1 + \frac{1}{NT} \sum_{n=-\infty}^{\infty} G(stjn\omega_s) H(stjn\omega_s)} \end{aligned}$$

Sampled PLL Analysis : Z-Transforms [5]

Type I

$$G_{OL}(z) = \frac{K}{z-1} ; \quad K = \frac{K_d K_v T}{N} \quad (\text{Ideal Loop})$$

$$\theta_e(nT) = \frac{2\pi \Delta f}{K_d K_v} \left[1 - (1-K)^n \right] \quad \text{Radians}$$

$$\text{Gain Margin} = -20 \log \left(\pi \frac{\omega_N}{\omega_s} \right) ; \quad \omega_N = \frac{K_d K_v}{N}$$

For $K \approx 1$, Gain Margin = 6 db

(Exclusion of high order components re aliasing would predict gain margin 13.1 db)

Sampled PLL Analysis [5]

Type II

$$G_{OL}(z) = \frac{K_d K_v T \left\{ \left[\frac{T}{2} + \gamma_2 \right] z + \left[\frac{T}{2} - \gamma_2 \right] \right\}}{N \gamma_1 (z-1)^2}$$

$$\theta_e(nT) = \frac{2\pi f T}{a-b} \left[a^n - b^n \right]$$

$$a, b = \frac{-A \pm \sqrt{A^2 - 4B}}{2}$$

$$A = 2 - K \frac{T/2 + \gamma_2}{\gamma_1}$$

$$B = 1 + K \frac{T/2 - \gamma_2}{\gamma_1}$$

$$K = \frac{K_d K_v T}{N}$$

$$\text{Gain Margin} = -20 \log \left[2\pi \frac{\omega_N}{\omega_s} \right] \quad \omega_N^2 = \frac{K_d K_v}{N \gamma_1}$$

$$= 2.5 \text{ db for speed-optimized PLL}$$

Sampled PLL Analysis [6]

Type II with Internal Time Delay

$$G_{OL}(z) = \frac{\omega_n^2 (a z^2 + b z + c)}{(z-1)^3}$$

$$\Theta_e(z) = \frac{\Delta\theta z^3 + (2\pi\Delta f T - \Delta\theta) z^2}{z^3 + z^2(a\omega_n^2 - 2) + z(1 + b\omega_n^2) + \omega_n^2 c}$$

$$\omega_n^2 = \frac{K_d K_v}{N \tau_1}$$

$\Delta\theta$ = phase error step, Rad.

Δf = frequency step, Hz


$$m = 1 - \tau_{\text{delay}}/T$$

$$a = \frac{(mT)^2}{2} + mT\tau_2$$

$$b = \frac{T^2}{2} (2m - 2m^2 + 1) - 2m\tau_2 T + \tau_2 T$$

$$c = \frac{T^2}{2} (m-1)^2 + \tau_2 (m-1)T$$

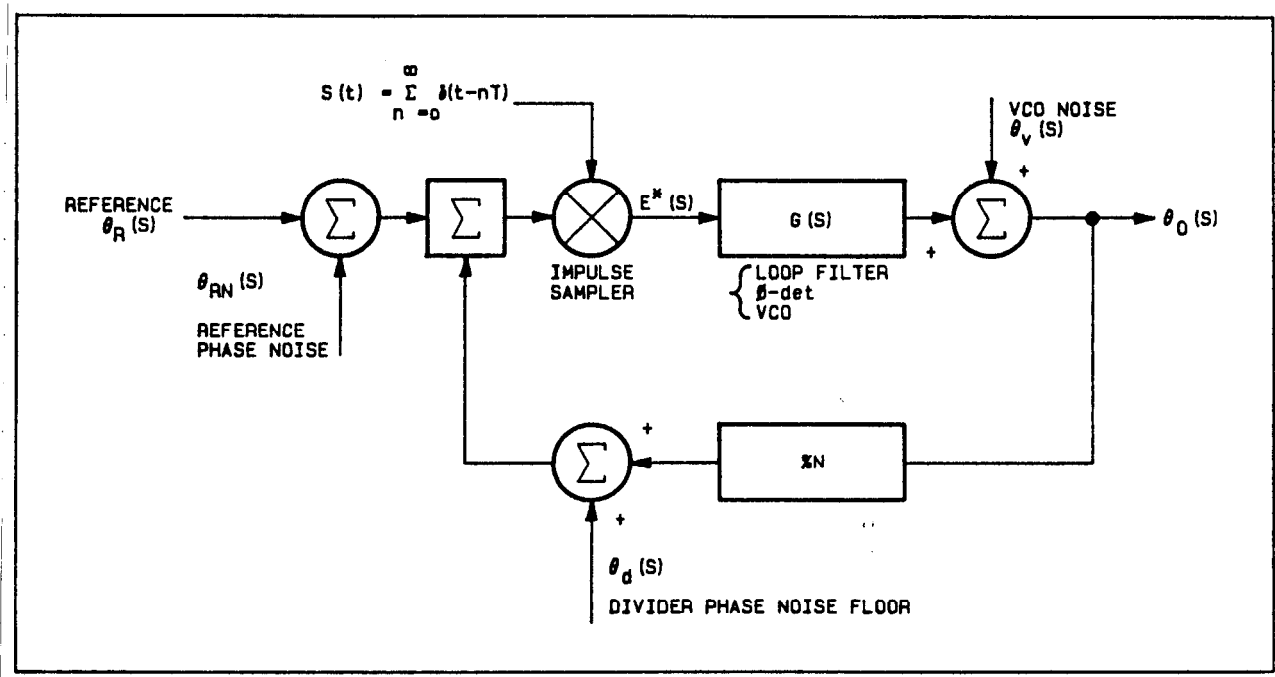Sampled PLLs: Phase Noise Considerations [5]



Phase Noise [s]

Reference noise effect upon the output phase noise:

$$\theta_o(s) \Big|_{\text{Ref}} = \frac{\theta_{RN}^*(s) G(s)}{1 + \frac{G^*(s)}{N}}$$

Divider noise effect upon the output phase noise:

$$\theta_o(s) \Big|_{\text{Div}} = \frac{\theta_d^*(s) G(s)}{1 + \frac{G^*(s)}{N}}$$

VCO noise effect upon the output phase noise spectrum:

$$\theta_o(s) \Big|_{\text{VCO}} = \frac{\theta_v(s) + \left[\theta_v(s) G^*(s) - \theta_v^*(s) G(s) \right] / N}{1 + \frac{G^*(s)}{N}}$$

Not necessarily 0

$$\approx \frac{\theta_v(s)}{1 + \frac{G^*(s)}{N}}$$

Simplified Phase Noise : (Type I Loop Only, Ideal) [s]

Reference Noise

$$\frac{S_o(\omega)}{S_{RN}(\omega)} = \frac{16 K^2 N^2 \sin^4(\omega T/2)}{(\omega T)^4 (K^2 + 2 - 2K + 2(K-1)\cos(\omega T))} \quad ; K = \frac{K_d K_v T}{N}$$

$$= N^2 \left[\frac{\sin(\omega T/2)}{(\omega T/2)} \right]^4 \quad \text{for } K \equiv 1$$

Divider Noise

Same as reference case

VCO Noise

$$\frac{S_o(\omega)}{S_v(\omega)} = \frac{4 \sin^2(\omega T/2)}{K^2 + 2 - 2K + 2(K-1)\cos(\omega T)}$$

$$= 4 \sin^2\left(\frac{\omega T}{2}\right) \quad \text{for } K \equiv 1$$

Practical Considerations

- * Power Supply Filtering
- * Post-Tuning Drift
- * Feedback Dividers
- * Phase Noise Considerations
- * Non-ideal Features
 - VCO linearity
 - Sampling Efficiency
 - Transport Delay

References

1. Gardner F.M. Phaselock Techniques
 2. Viterbi A.J. Principles of Coherent Communications
 3. Leeson D.B. "A Simple Model of Feedback Oscillator Noise Spectrum" *IEEE Proc.* Feb 1966
 4. Cutler L.S. "Some Aspects of the Theory and Measurement of Frequency Fluctuations in Frequency Standards" *IEEE Proc.* Feb. 1966
 5. Crawford J.A. "Understanding the Specifics of Sampling in Synthesis" *Microwaves & RF* Aug., Sept. 1984
 6. Crawford J.A. "Frequency Synthesizer IR & D" *TRW IOC C423.25-85* May 23, 1985
-
7. Ward C.J. "Delay Reduction Techniques in Phase-Locked Loop Amplifiers" *Electronic Letters* Apr. 2, 1981
 8. Crawford J.A. "Frequency Synthesizer IR & D" *TRW IOC C423.25-91* June 5, 1985
 9. Crawford J.A. "Universal L/X Band Frequency Synthesizer" *TRW IOC C423.25-94* July 9, 1985
 10. Baugh R.A. "Low Noise Frequency Multiplication" *Frequency Control Symposium*
 11. Andresen S.G. "Phase Noise of Various Frequency Doublers" *IEEE IM-22* June, 1973

12. Egan W.F. "The Effects of Small Contaminating Signals in Nonlinear Elements Used in Frequency Synthesis & Conversion" *IEEE Proc.* July, 1981
13. Rotholz E. "Phase Noise of Mixers" *Electronic Letters* 13 Sept. 1984
14. Kroupa V.F. "Noise Properties of PLL Systems" *IEEE COM-30* Oct. 1982
15. Walls F.L. et al "Design Considerations in State-of-the-Art Signal Processing and Phase Noise Measurement Systems" *Frequency Control Symposium* 1976
16. Peregrino L. "Phase Noise Measurement Using a High Resolution Counter with on-Line Data Processing" *Frequency Control Symposium*
17. Noordanus J. et al "Direct-division Phase-Lock Loop at 12 GHz" *IEE Proc.* Dec. 1983
18. Goldwasser W.J. "Design Shortcuts for Microwave Frequency Dividers" *Electronic Engineer* May, 1970
19. Upadhyayula L.C. "Microwave Frequency Dividers" *RCA Review* Dec. 1973
20. Harrison R.G. "A Broad-Band Frequency Divider Using Microwave Varactors" *IEEE MTT-25*, Dec. 1977