

<b>Title:</b>	RPAD- Resistive Attenuator Design
<b>Author:</b>	J.A. Crawford for AM1 LLC
<b>Abstract:</b>	This brief memo provides technical back-up to the RPAD computer program.
<b>Date:</b>	16 July 2011
<b>Version:</b>	1.0

## 1 Introduction

Impedance-matched resistive attenuator design is fundamentally based on the theory of image parameter filters as discussed in §6.2 of [1]. When properly designed, each port of the attenuator provides an ideal impedance match at each respective port.

Given the desired input and output port impedances represented by  $R_{in}$  and  $R_{out}$  respectively, the minimum attenuator gain that can be realized under the matched condition is given by

$$A_{\min} = \frac{20}{2.3026} \cosh^{-1} \left( \sqrt{\frac{R_{in}}{R_{out}}} \right) \quad \text{dB} \quad (1)$$

where it has been assumed that  $R_{in} \geq R_{out}$ .

The design equations for the tee-attenuator shown in Figure 1 are as follows:

$$\begin{aligned} R_2 &= \frac{\sqrt{R_{in} R_{out}}}{\sinh(A_{np})} \\ R_1 &= R_2 \left[ \sqrt{\frac{R_{in}}{R_{out}}} \cosh(A_{np}) - 1 \right] \\ R_3 &= R_2 \left[ \sqrt{\frac{R_{out}}{R_{in}}} \cosh(A_{np}) - 1 \right] \end{aligned} \quad (2)$$

and  $A_{np}$  is the desired power attenuation factor in units of nepers. Given the desired attenuation  $A_{dB}$  in dB,

$$A_{np} = \frac{2.3026}{20} A_{dB} \quad (3)$$

The design equations for the  $\pi$ -attenuator shown in Figure 2 are similarly given by

$$\begin{aligned} R_2 &= \sqrt{R_{in} R_{out}} \sinh(A_{np}) \\ R_1 &= R_2 \left[ \sqrt{\frac{R_{out}}{R_{in}}} \cosh(A_{np}) - 1 \right]^{-1} \\ R_3 &= R_2 \left[ \sqrt{\frac{R_{in}}{R_{out}}} \cosh(A_{np}) - 1 \right]^{-1} \end{aligned} \quad (4)$$

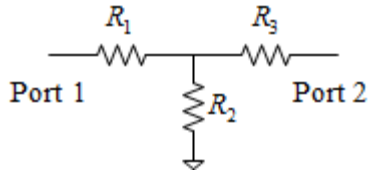
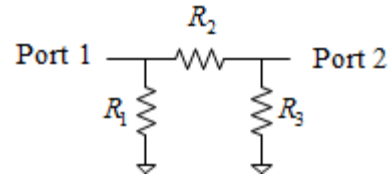


Figure 1 Tee resistive attenuator

Figure 2  $\pi$  resistive attenuator

## 2 Resultant Characteristics

Since resistors are normally only available in discrete values, it is helpful to compute the resultant attenuator performance once these real-world values have been selected. This can be done in a number of ways by using  $z$ -,  $y$ -, or  $ABCD$ - parameters. The method adopted here is the latter.

The  $ABCD$  matrices for the two attenuator types are given by [2]

$$\begin{aligned} \begin{bmatrix} A & B \\ C & D \end{bmatrix}_{\pi} &= \begin{bmatrix} 1 & 0 \\ R_1^{-1} & 1 \end{bmatrix} \begin{bmatrix} 1 & R_2 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ R_3^{-1} & 1 \end{bmatrix} \\ &= \begin{bmatrix} \left(1 + \frac{R_2}{R_3}\right) & (R_2) \\ \left(R_1^{-1} + R_3^{-1} + \frac{R_2}{R_1 R_3}\right) & \left(1 + \frac{R_2}{R_1}\right) \end{bmatrix} \end{aligned} \quad (5)$$

$$\begin{aligned} \begin{bmatrix} A & B \\ C & D \end{bmatrix}_{tee} &= \begin{bmatrix} 1 & R_1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ R_2^{-1} & 1 \end{bmatrix} \begin{bmatrix} 1 & R_3 \\ 0 & 1 \end{bmatrix} \\ &= \begin{bmatrix} \left(1 + \frac{R_1}{R_2}\right) & \left(R_1 + R_3 + \frac{R_1 R_3}{R_2}\right) \\ R_2^{-1} & \left(1 + \frac{R_3}{R_2}\right) \end{bmatrix} \end{aligned} \quad (6)$$

Given these results, it is a simple matter to compute the corresponding S-parameters from the following relationships:

$$S_{11} = \frac{AR_{out} + B - CR_{in}R_{out} - DR_{in}}{d} \quad (7)$$

$$S_{12} = \frac{2(AD - BC)\sqrt{R_{in}R_{out}}}{d} \quad (8)$$

$$S_{21} = \frac{2\sqrt{R_{in}R_{out}}}{d} \quad (9)$$

$$S_{22} = \frac{-AR_{out} + B - CR_{in}R_{out} + DR_{in}}{d} \quad (10)$$

where

$$d = AR_{out} + B + CR_m R_{out} + DR_{in} \quad (11)$$

### 3 Design Example Using RPAD

Assume that a 10 dB  $\Omega$ -attenuator pad is desired between a source impedance of 50 $\Omega$  and a load impedance of 75 $\Omega$ . The parameters are entered into the program form as shown in Figure 3 followed by clicking on the *Calculate* button. As also shown, the minimum possible attenuation possible between these two port impedances is 5.72 dB. The user has a choice to select between 1%, 5%, or 10% standard resistor values and all of the nearest-neighbor resistor values permuted as shown. The user is free to select which attenuator design meets their requirements better.

**RPad**  
Resistive Attenuator Design  
Copyright 2011 AM1 LLC

Pi  
 Tee

Port 1: Source Impedance, Ohms    
Port 2: Load Impedance, Ohms

Minimum Attenuation, dB (Amin)

Desired Attenuation, dB (0.01 to 60)

Resistor Tolerance  1%  5%  10%

Exact R Values  \*\*\*Valid\*\*\*

Nearest Resistor Value Permutations					
R1	R2	R3	S11(dB)	S22(dB)	S21(dB)
76.80	86.60	205.00	-53.23	-48.53	-10.00
76.80	86.60	210.00	-55.17	-64.47	-9.96
76.80	88.70	205.00	-68.01	-54.39	-10.11
76.80	88.70	210.00	-61.68	-44.01	-10.07
78.70	86.60	205.00	-44.87	-50.60	-9.93
78.70	86.60	210.00	-44.22	-57.10	-9.90
78.70	88.70	205.00	-41.59	-51.43	-10.04
78.70	88.70	210.00	-41.15	-43.00	-10.00

Figure 3 Design example using RPAD

### 4 References

1. Giacoletto, L.J., *Electronics Designers' Handbook*, 2<sup>nd</sup> ed., McGraw-Hill Book, 1977.
2. Davis, W. Alan, *Microwave Semiconductor Circuit Design*, Van Nostrand Reinhold, 1984.